

CSED311 Lab2: RTL Design

Junho Lee

jjunho2@postech.ac.kr



Contents


- Combinational logic
- Register-Transfer Level
- Finite State Machine
- Assignment



Combinational logic

- Represents Boolean function (time-independent)
- Output is a function of inputs only
- $\text{output} = f(\text{input})$

- Example: 4-to-1 mux

 

[3:0]in	sel	out
2'bxxx0	2'b00	0
2'bxxx1	2'b00	1
2'bxx0x	2'b01	0
2'bxx1x	2'b01	1
2'bx0xx	2'b10	0
2'bx1xx	2'b10	1
2'b0xxx	2'b11	0
2'b1xxx	2'b11	1



Combinational logic

- Implementation with Verilog (mux)

Using Assign	Using Always
<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; assign out = (sel == 2'b00) ? in[0] : (sel == 2'b01) ? in[1] : (sel == 2'b10) ? in[2] : in[3]; endmodule</pre>	<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; reg out; always @ (sel or in) begin if (sel == 2'b00) out <= in[0]; else if (sel == 2'b01) out <= in[1]; else if (sel == 2'b10) out <= in[2]; else out <= in[3]; end endmodule</pre>




Register-Transfer Level

- The design method to implement a **synchronous circuit** with a HDL (Hardware Description Language)
- Synchronous circuit consists of:
 - **Register**: a memory element synchronized by the clock signal
 - **Combinational logic**: logical function



RTL - example

- Toggler example

 

<Fig 1. "Register transfer level - example toggler" (Register-transfer level, Wikipedia, https://en.wikipedia.org/wiki/Register-transfer_level)>

```
module toggler(input clk, output out);  
    reg state;  
    wire comb;  
  
    assign comb = ~state;  
    assign out = state;  
  
    initial begin  
        state <= 0;  
    end  
  
    always @(posedge clk) begin  
        state <= comb;  
    end  
endmodule
```




Finite State Machine (FSM)

- Moore machine
- Mealy Machine




Finite State Machine (FSM)

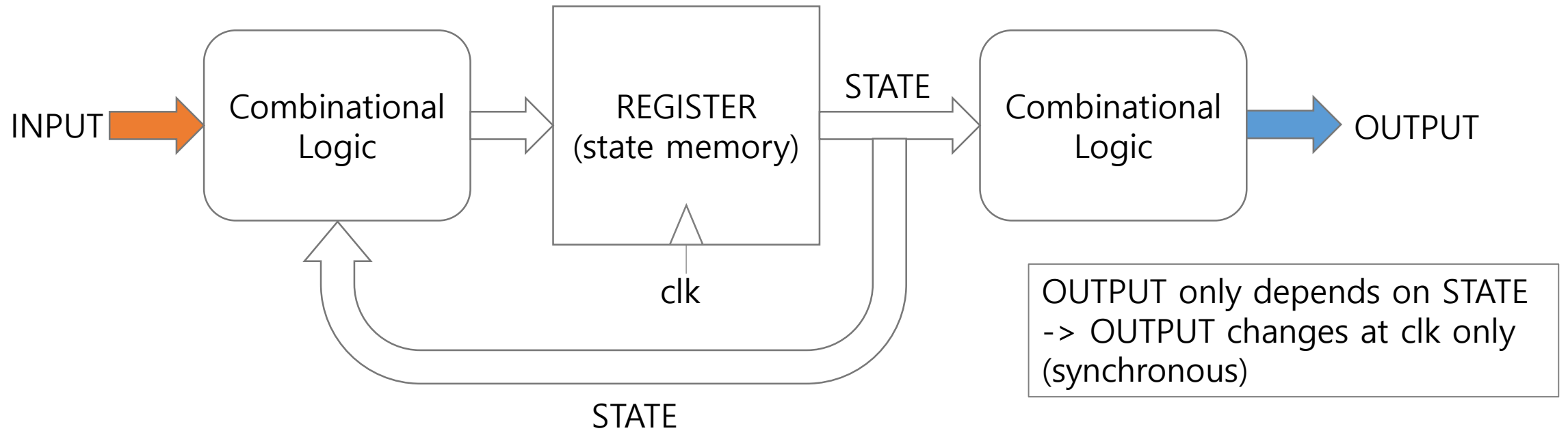- Moore Machine
 - Outputs only depend on the current state.




Finite State Machine (FSM)

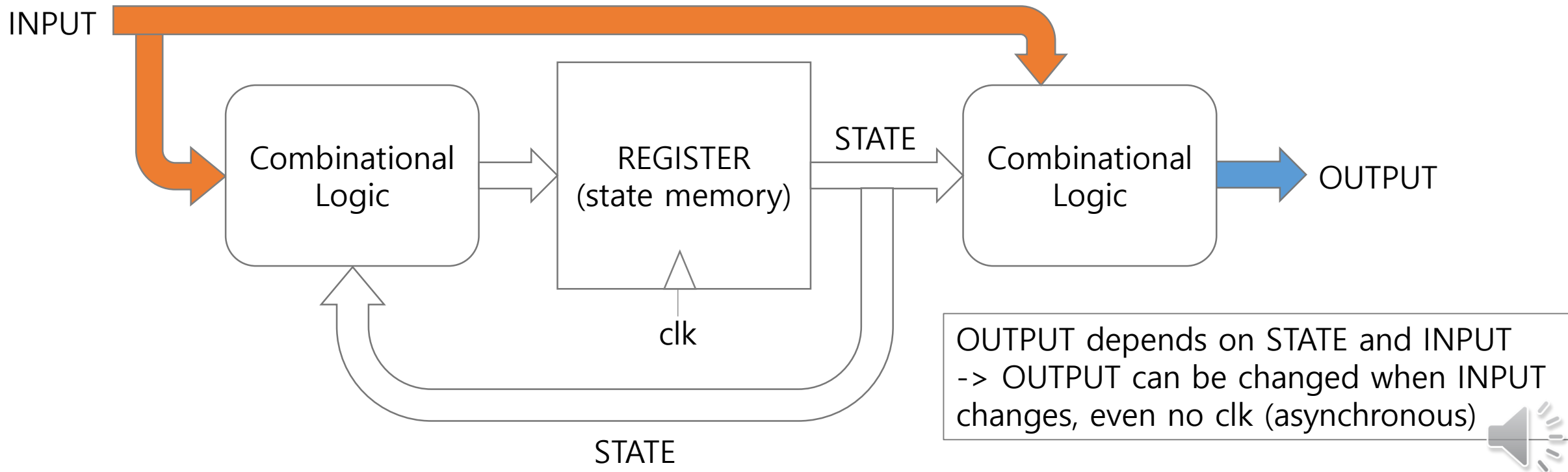- Mealy Machine
 - Outputs depend on the current state and the current inputs




Finite State Machine (FSM)

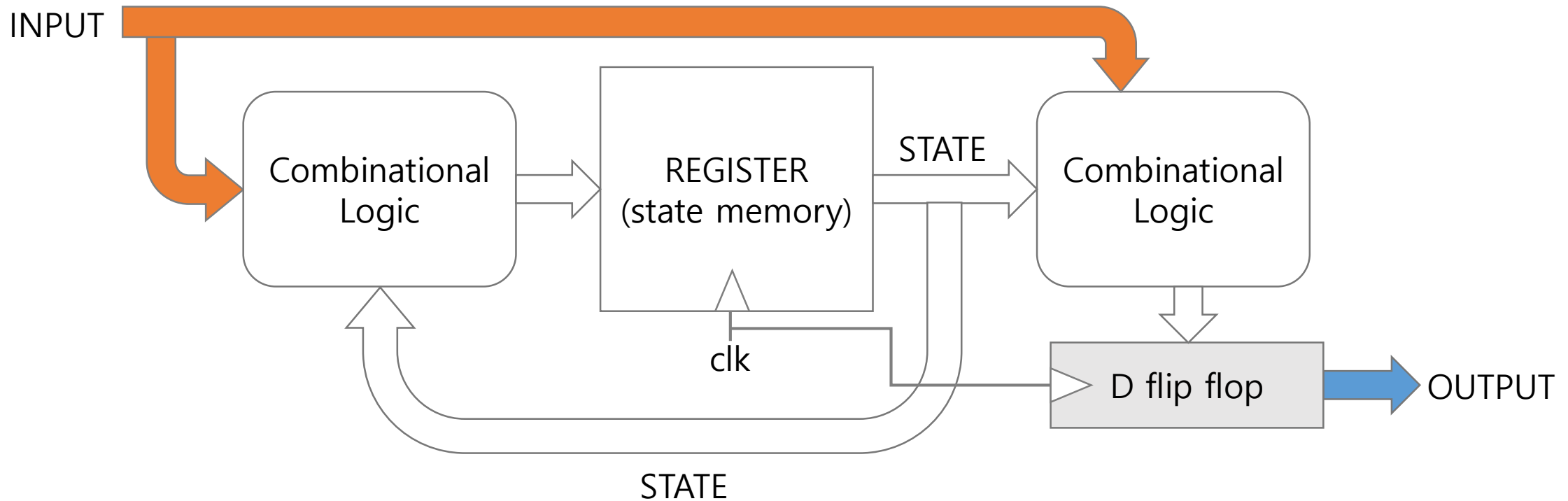- Mealy Machine
 - Mealy Machine can be made synchronous




FSM Code Structure

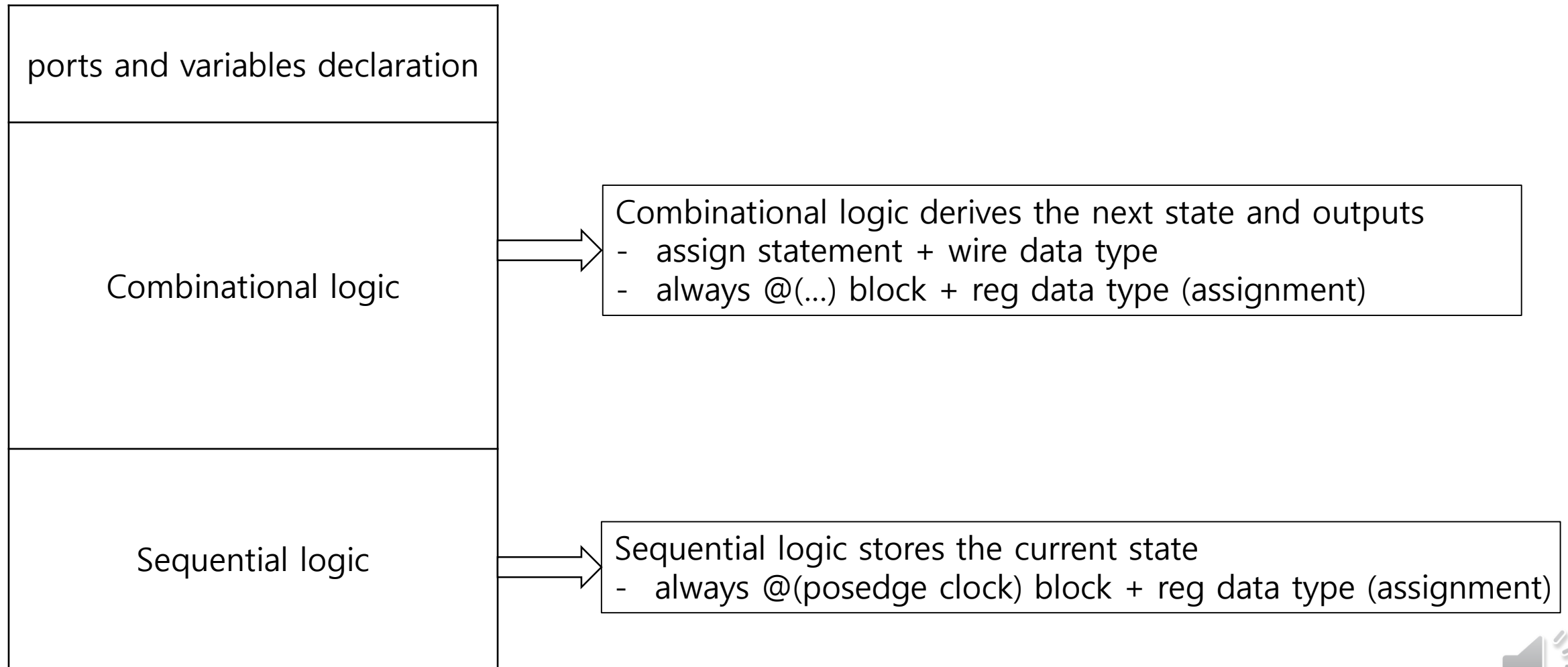

FSM Code Structure

❖ Example: Mealy Machine

 

Output: reg →

Example: Reduce 1's

Given a sequence of 0s and 1s, *change the first 1 of consecutive 1s into 0*

Examples:

0000**111**00 -> 0000**011**00

0**10101010** -> 0**00000000**

0**11001100** -> 0**01000100**

NS & Output
Calculation

CS
Calculation

```
module mealy (Clock, w, Resetn, z);
  input Clock, w, Resetn ;
  output reg z ;
  reg CS, NS;
  parameter A = 1'b0, B = 1'b1;
  always @(w, CS)
    case (CS)
      A: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 0;
          end
      B: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 1;
          end
    endcase
  always @(posedge Clock, negedge Resetn)
    if (Resetn == 0)
      CS <= A;
    else
      CS <= NS;
endmodule
```

Combinational
(Blocking)

Sequential
(Non-Blocking)

z is output and z is in combinational logic part
-> asynchronous Mealy Machine



Assignment

- Implement a simple vending machine RTL in Verilog
 - A simple Finite State Machine (FSM)
- Your vending machine should cover all use-cases (in the next slides)
- A skeleton code and testbench will be provided.
- Submit a report and code to LMS
 - Due date
 - Code: 2020. 4. 6 / 9:00 am
 - Report: 2020. 4. 6 / 8:00 pm
 - Demo
 - 2020. 4. 6~7 8:00 pm ~ 10:00 pm



Assignment

- Vending machine interface

INPUT		
Signal	Description	Number of bit(s)
i_input_coin	Insert Coin	1 for each type of coins
i_select_item	Select Item	1 for each type of items
i_return_trigger	Return change	1
clk	clock	1
reset_n	reset	1

OUTPUT		
Signal	Description	Number of bit(s)
o_output_item	Indicate dispensed items	1 for each type of items
o_available_item	Indicate item availability	1 for each type of item
o_return_coin	Indicate type of coin (change)	1 for each type of coins



Assignment

- Vending machine use-case

Assumption: infinite item, change

Sequence

1. Insert money (available money unit: 100, 500, 1000 won)
2. Vending machine shows all available items where (item cost \leq current money && item count > 0)
- 3.a. Insert money within waiting time
 - 3.a.1. Go to 2
- 3.b. Select an item within waiting time
 - 3.b.a. Case1: the item is available
 - 3.b.a.1. The item is dispensed
 - 3.b.a.2. Go to 2
 - 3.b.b. Case 2: the item is unavailable
 - 3.b.b.1. Nothing happens. Waiting time is not reset.
- 3.c. No input within waiting time
 - 3.c.1 Return changes
- a*. Whenever press the return button
 - a*.1. Return changes
 - a*.2. Go to 1



Assignment

- Submission
 - Submit your assignment to LMS with filename:
 - Lab2_{TeamID}_{StudentID1}_{StudentID2}.pdf
 - PDF file of your report
 - Lab2_{TeamID}_{StudentID1}_{StudentID2}.zip
 - Zip file of your code (*.v)



Assignment tips

- If your modelsim is not displaying the output of \$display or \$monitor, then try using vending_machine_tb_f.v. (output will be written to output.txt)
- If your simulation keeps running, the testbench module is waiting for the output signals. (o_output_item or o_return_coin)
- If your vending machine code passes all tests, you will get the message "Passed = 10, Failed = 0".



Assignment tips

- #1:** When modeling sequential logic, use nonblocking assignments.
- #2:** When modeling latches, use nonblocking assignments.
- #3:** When modeling combinational logic with an always block, use blocking assignments.
- #4:** When modeling both sequential and combinational logic within the same always block, use nonblocking assignments.
- #5:** Do not mix blocking and nonblocking assignments in the same always block.
- #6:** Do not make assignments to the same variable from more than one always block.
- #7:** Use \$strobe to display values that have been assigned using nonblocking assignments.
- #8:** Do not make assignments using #0 delays.



Announcement

- If you have any problem, contact TAs with following options
 - Microsoft Teams – Lab QnA channel
 - Mail – TA alias ("csed311-ta")
 - LMS – Question Board



Reference

- "Register-transfer level", Wikipedia, last modified Jan 24, 2019, accessed Mar 03, 2019, https://en.wikipedia.org/wiki/Register-transfer_level
- http://www.sunburst-design.com/papers/CummingsSNUG2000SJ_NBA.pdf

